



University of Science and Technology

Electronic engineering



Tutorial of Physics II

COURSE COORDINATOR

Lecturer: Dr. Alzubair Jaafer

Current, Resistance, and Ohm's Law

A CURRENT (I)

$$I = \frac{q}{t}$$

amperes ($1 \text{ A} = 1 \text{ C/s}$).

A BATTERY is a source of electrical energy

the terminal potential difference of a battery is equal to its emf.

The unit for emf is the same as the unit for potential difference, the volt.

THE RESISTANCE (R)

$$R = \frac{V}{I} \quad 1 \Omega = 1 \text{ V/A}.$$

OHM'S LAW Ohm also stated that R is a constant independent of V and I .

THE TERMINAL POTENTIAL DIFFERENCE

current I is related to its electromotive force $\mathcal{E}$ and its *internal resistance* r as follows:

(1) When delivering current (*on discharge*):

Terminal voltage = (emf) – (voltage drop in internal resistance)

$$V = \mathcal{E} - Ir$$

(2) When receiving current (*on charge*):

Terminal voltage = emf + (voltage drop in internal resistance)

$$V = \mathcal{E} + Ir$$

(3) When no current exists:

Terminal voltage = emf of battery or generator

RESISTIVITY:

$$R = \rho \frac{L}{A}$$

L in m, A in m^2 , and R in Ω , the units of ρ are $\Omega \cdot \text{m}$.

RESISTANCE VARIES WITH TEMPERATURE:

$$R = R_0 + \alpha R_0 (T - T_0)$$



units of α K^{-1} or $^{\circ}\text{C}^{-1}$.

$$\rho = \rho_0 + \alpha \rho_0 (T - T_0)$$



POTENTIAL CHANGES:


The potential difference across a resistor R

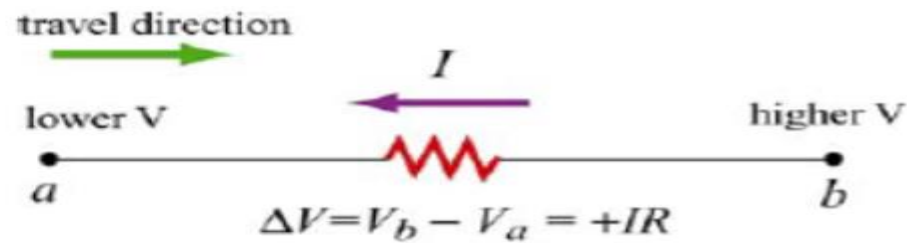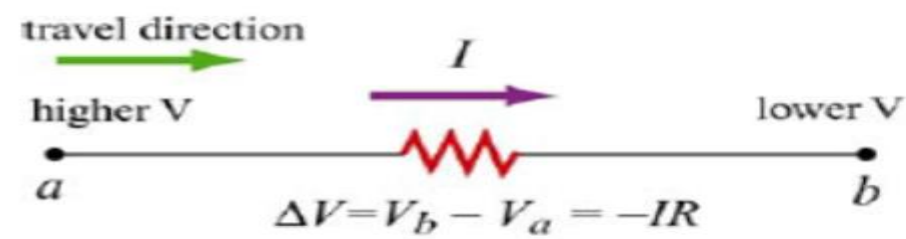Current always flows “downhill,” from high to low potential, through a resistor.



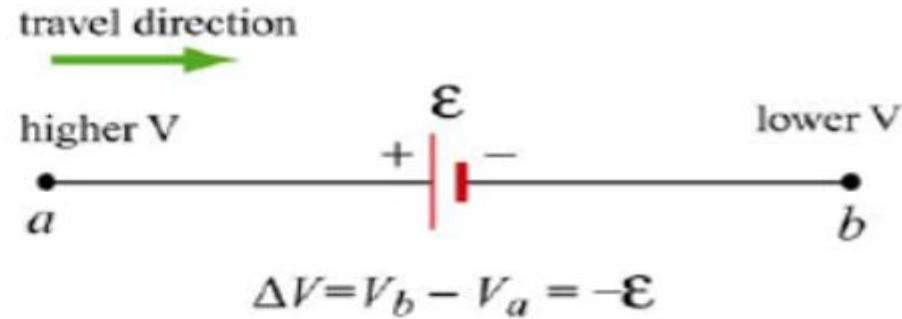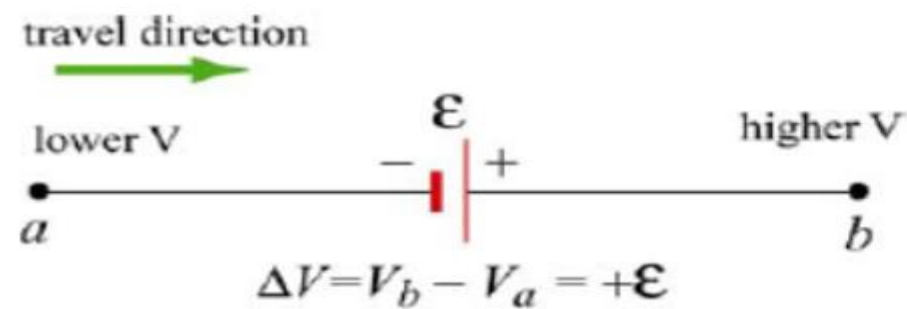
The positive terminal of a battery is always the high-potential



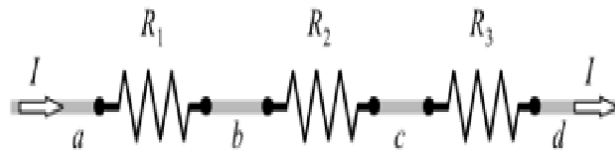

$$R_{\text{eq}} = R_1 + R_2 + R_3 + \dots \quad (\text{series combination})$$

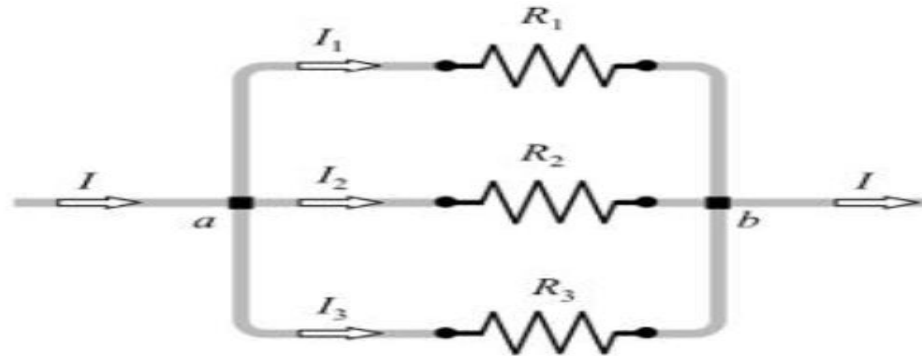
The equivalent resistance in series is always greater than the largest of the individual resistances.



$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots \quad (\text{parallel combination})$$

The equivalent resistance in parallel is always less than the smallest of the individual resistances.

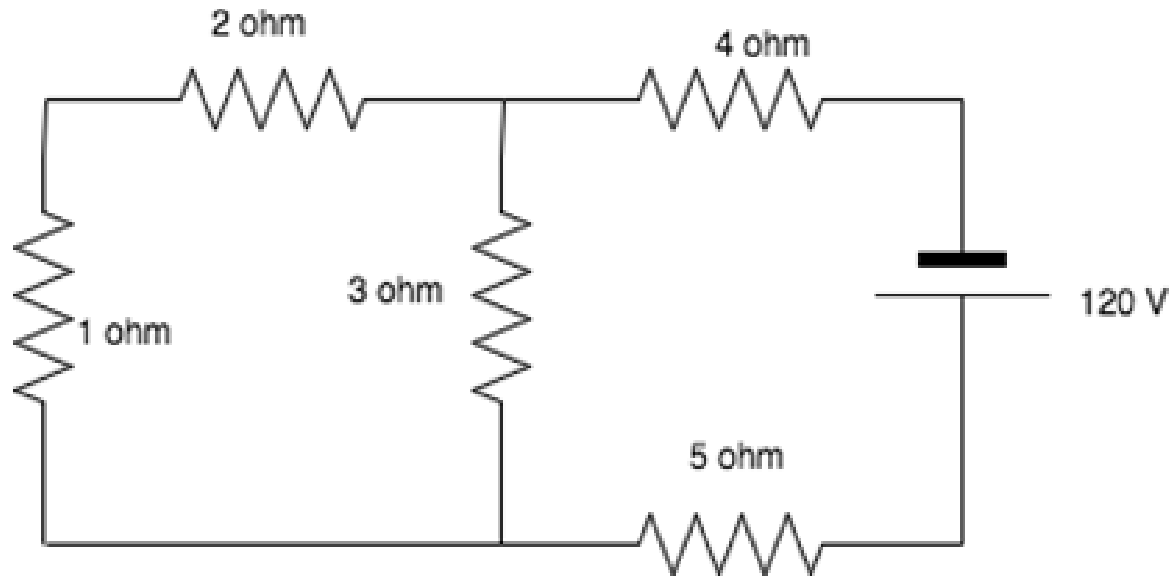Calculate the total current in the circuit.



$$1 \text{ and } 2 \text{ in series} = 1 + 2 = 3\Omega$$

$$3 \text{ and } 3 \text{ in parallel} = \frac{1}{3} + \frac{1}{3} = \frac{2}{3} \therefore \frac{3}{2} = 1.5\Omega$$

$$1.5, 4 \text{ and } 5 \text{ in series} = 1.5 + 4 + 5 = 10.5\Omega$$

$$I = \frac{120}{10.5} = 11.4287\text{A} = 11.43\text{A}$$

How many electrons per second pass through a section of wire carrying a current of 0.70 A?

Ans. 4.4×10^{18} electrons/s

Solution:

$$q = It = 1 \times 0.7 = 0.7C$$

$$NO = \frac{q}{e} = \frac{0.7}{1.6 \times 10^{-19}} = 0.4375 \times 10^{-19} = 4.4 \times 10^{18} \text{ e}\backslash s$$

An electron gun in a TV set shoots out a beam of electrons. The beam current is 1.0×10^{-5} A. How many electrons strike the TV screen each second? How much charge strikes the screen in a minute?

Ans. 6.3×10^{13} electrons/s, -6.0×10^{-4} C/min

Solution:

$$q = It = 1 \times 10^{-5} \times 1 = 1 \times 10^{-5}C$$

$$NO = \frac{q}{e} = \frac{1 \times 10^{-5}}{1.6 \times 10^{-20}} = 0.0625 \times 10^{20-5} = 0.0625 \times 10^{15} = 6.3 \times 10^{13} \text{ e}]s$$

$$q = It = 1 \times 10^{-5} \times 60 = 6 \times 10^{-4}C\backslash min$$

What is the current through an $8.0\text{-}\Omega$ toaster when it is operating on 120 V ? *Ans.* 15 A

Solution:

$$I = \frac{V}{R} = \frac{120}{8} = 15\text{A}$$

What potential difference is required to pass 3.0 A through $28\text{ }\Omega$? *Ans.* 84 V

Solution:

$$V = IR = 3 \times 28 = 84\text{ V}$$

Determine the potential difference between the ends of a wire of resistance $5.0\text{ }\Omega$ if 720 C passes through it per minute. *Ans.* 60 V

Solution:

$$I = \frac{q}{t} = \frac{720}{60} = 12\text{A}$$

$$V = IR = 12 \times 5 = 60\text{ V}$$

Find the potential difference between points A and B in Fig. 26-5 if R is $0.70\ \Omega$. Which point is at the higher potential? *Ans.* -5.1 V , point A



Solution:

$$(V_A - V_B) = -6 - 2 \times 3 + 9 - 3 \times 0.7 = -6 - 6 + 9 - 2.1 = -5.1\text{ V}$$

+A is high and - B is low

Compute the resistance of 180 m of silver wire having a cross-section of 0.30 mm^2 . The resistivity of silver is $1.6 \times 10^{-8}\ \Omega \cdot \text{m}$. *Ans.* $9.6\ \Omega$

Solution:

$$R = \rho \frac{L}{A}$$

$$L = 180\text{ m}, \quad A = 0.3 \times 10^{-6}\text{ m}^2 \quad \rho = 1.6 \times 10^{-8}\ \Omega \cdot \text{m}$$

$$R = \frac{1.6 \times 10^{-8} \times 180}{0.3 \times 10^{-6}} = \frac{1.6 \times 180}{0.3} \times 10^{-8+6} = 960 \times 10^{-2}\ \Omega = 9.6\ \Omega$$

A coil of wire has a resistance of $25.00\ \Omega$ at 20°C and a resistance of $25.17\ \Omega$ at 35°C . What is its temperature coefficient of resistance? *Ans.* $4.5 \times 10^{-4}^\circ\text{C}^{-1}$

Solution:

$$R = R_0 + \alpha R_0(T - T_0)$$

$$R = R_0 (1 + \alpha(T - T_0))$$

$$\frac{R}{R_0} - 1 = \alpha(T - T_0)$$

$$\frac{25.17}{25} - 1 = \alpha(35 - 20)$$

$$0.0068 = 15\alpha$$

$$\alpha = \frac{0.0068}{15} = 4.533 \times 10^{-4}^\circ\text{C}^{-1} = 4.5 \times 10^{-4}^\circ\text{C}^{-1}$$

1. An electric current of 10 A is the same as _____

- a) 10 J/C
- b) 10 V/C
- c) 10C/sec
- d) 10 W/sec

2. Consider a circuit with two unequal resistances in parallel, then _____

- a) large current flows in large resistor
- b) current is same in both
- c) potential difference across each is same
- d) smaller resistance has smaller conductance

3. In which of the following cases is Ohm's law not applicable?

- a) Electrolytes
- b) Arc lamps
- c) Insulators
- d) Vacuum ratio values


4. Resistivity of a wire depends on _____

- a) length of wire
- b) cross section area
- c) material
- d) all of the mentioned

5. Give the SI unit of resistivity.

- a) ohm/metre²
- b) ohm metre²
- c) ohm meter
- d) ohm/meter

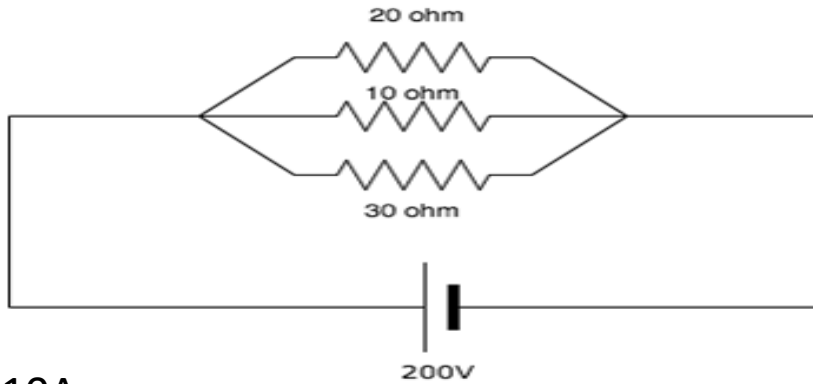6. Calculate the current across the 20 ohm [resistor](#).




- a) 10A
- b) 20A
- c) 6.67A
- d) 36.67A

7. In a parallel circuit, with a number of resistors, the voltage across each resistor is _____

- a) The same for all resistors
- b) Is divided equally among all resistors
- c) Is divided proportionally across all resistors
- d) Is zero for all resistors

8. The voltage across the open circuit is?

- a) 100V
- b) Infinity
- c) 90V
- d) 0V

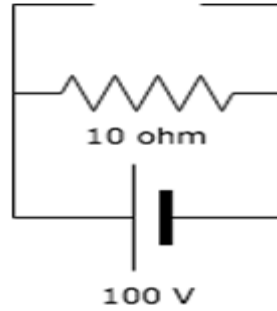


9. The currents in the three branches of a parallel circuit are 3A, 4A and 5A. What is the current leaving it?

- a) 0A
- b) Insufficient data provided
- c) The largest one among the three values
- d) 12A


10. Find the current in the circuit.

- a) 1 A
- b) 2 A
- c) 3 A
- d) 4 A

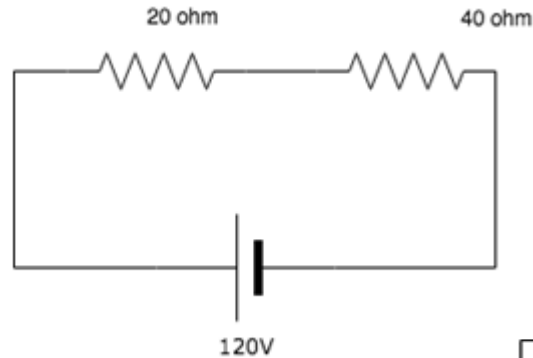

11. Voltage across the 60ohm resistor is_____

- a) 72V
- b) 0V
- c) 48V
- d) 120V

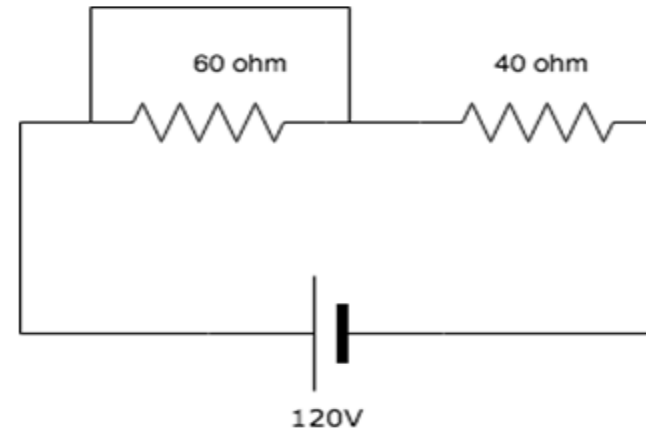

12. If there are two bulbs connected in series and one blows out, what happens to the other bulb?

- a) The other bulb continues to glow with the same brightness
- b) The other bulb stops glowing
- c) The other bulb glows with increased brightness
- d) The other bulb also burns out

13. What is the value of x if the current in the circuit is 5A?


- a) 15 ohm
- b) 25 ohm
- c) 55 ohm
- d) 75 ohm

14. What is the voltage measured across a series short?

- a) Infinite
- b) Zero
- c) The value of the source voltage
- d) Null

15. It is preferable to connect bulbs in series or in parallel?

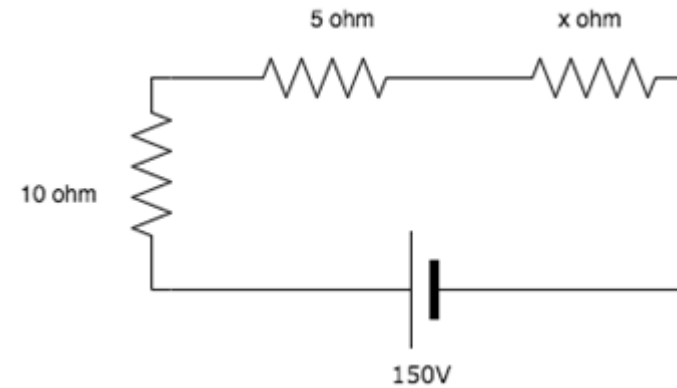- a) Series
- b) Parallel
- c) Both series and parallel
- d) Neither series nor parallel



16. Batteries are generally connected in _____

- a) Series
- b) Parallel
- c) Either series or parallel
- d) Neither series nor parallel

17. In a _____ circuit, the total resistance is greater than the largest resistance in the circuit.

- a) Series
- b) Parallel
- c) Either series or parallel
- d) Neither series nor parallel

18. In a _____ circuit, the total resistance is smaller than the smallest resistance in the circuit.

- a) Series
- b) Parallel
- c) Either series or parallel
- d) Neither series nor parallel

19. Calculate the equivalent resistance between A and B.

- a) 6.67 ohm
- b) 46.67 ohm
- c) 26.67 ohm
- d) 10.67 ohm

